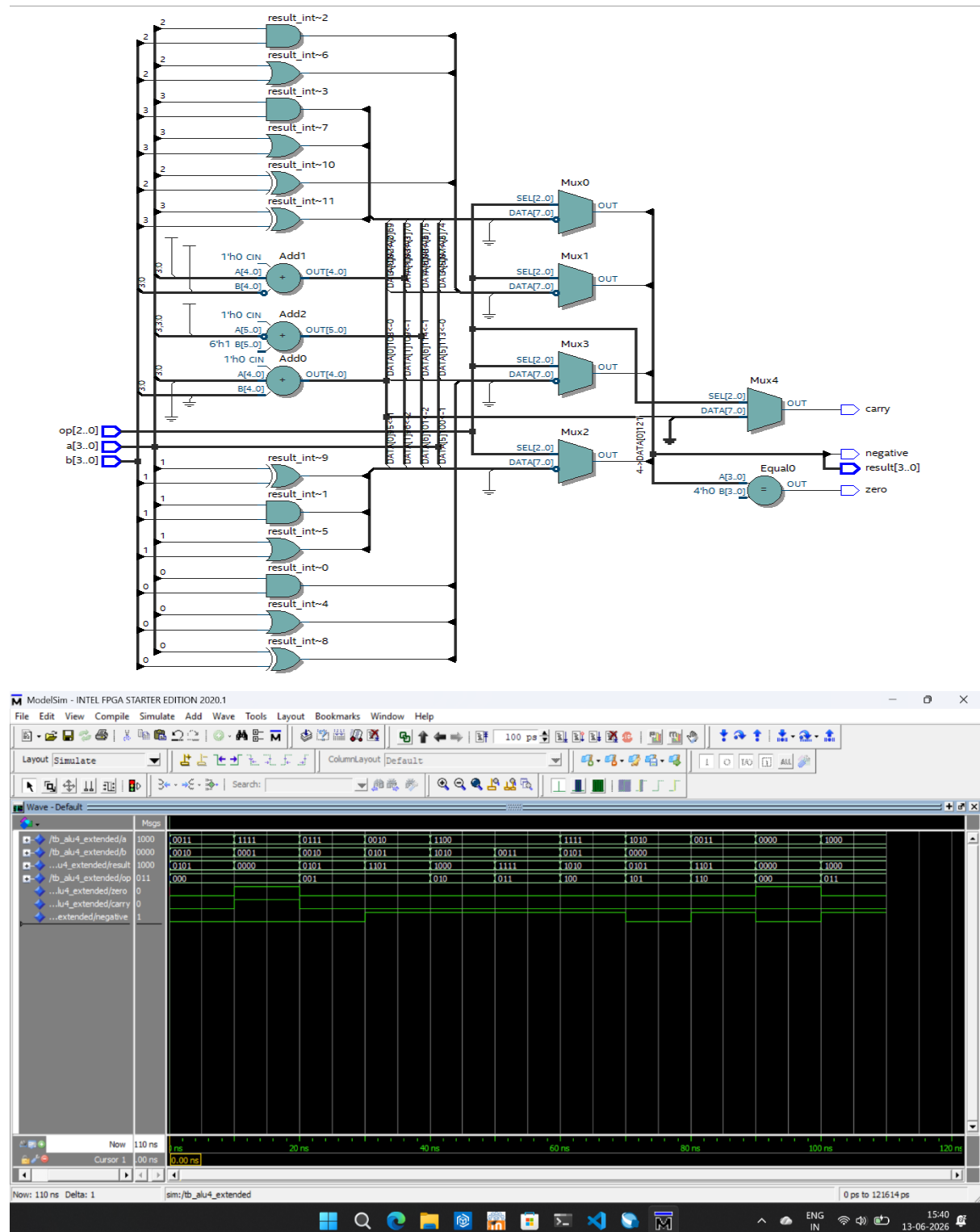


Washu2-CPU Week-4 Report



HARSHA VARDHAN

Alu4_extended:



Initially carry flag was always 0 because addition was performed using 4-bit operands, so overflow bit was discarded. Fixed by extending operands to 5 bits and extracting sum5(4) as carry.

Ram8x8:

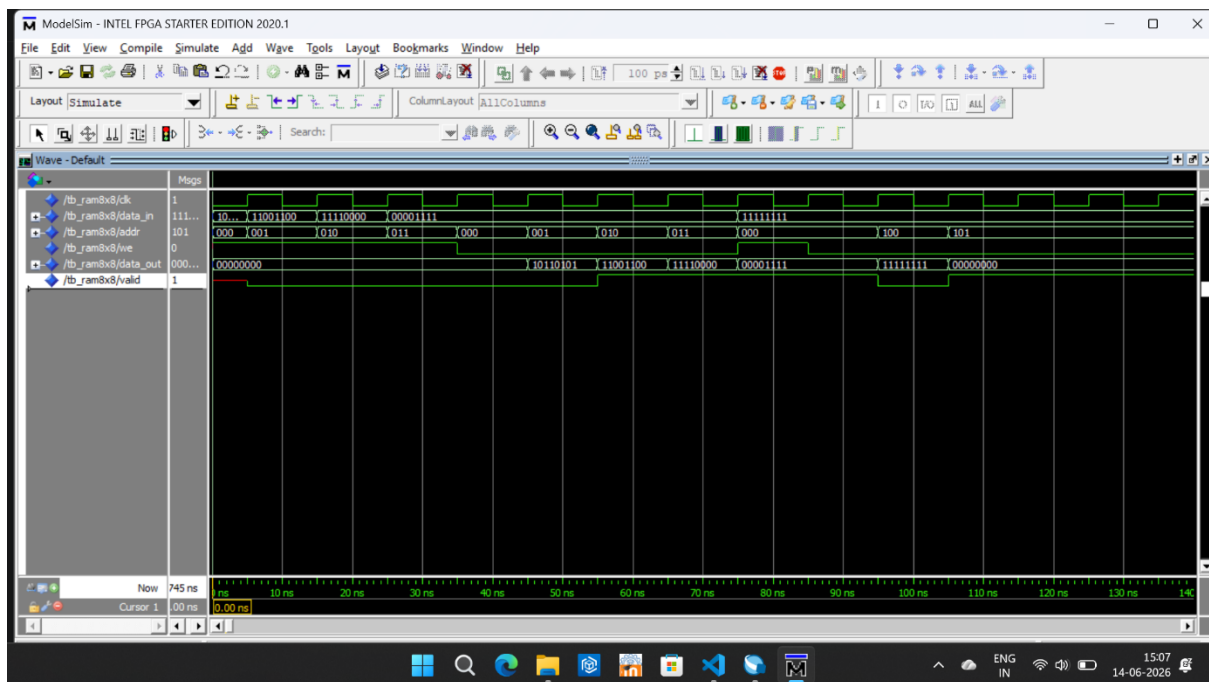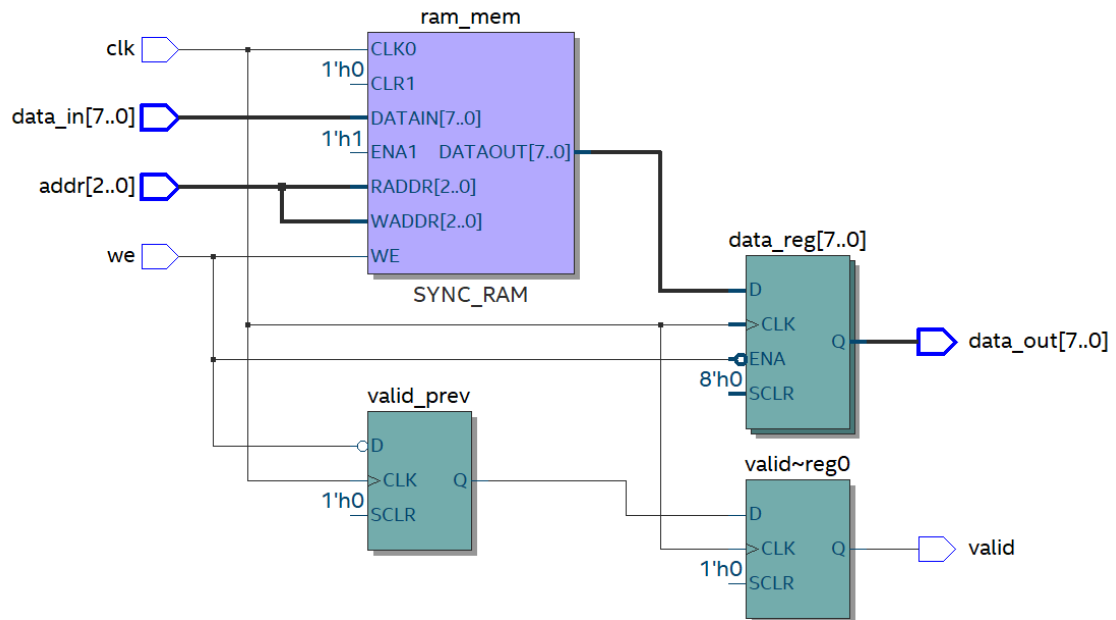

Initially **data_out** stayed undefined because the output port was connected in the wrong direction (**data_reg <= data_out**). Fixed by introducing an internal data register and driving **data_out <= data_reg**.